

EXPT NO. : 9

AIM:

To design and implement a BCD adder using IC 7483 and other logic gates.

APPARATUS REQUIRED:

Sl. No.	COMPONENT	SPECIFICATION	QTY.
1.	4-BIT BINARY FULL ADDER	IC 7483	2
2.	AND GATE	IC 7408	1
3.	OR GATE	IC 7432	1
4.	BREAD BOARD	-	1
5.	PATCH CORDS	-	-
6.	POWER SUPPLY WITH LOGIC PROBE	-	1

THEORY:


A BCD adder considers the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage. Since each input digit does not exceed 9, the output sum cannot be greater than 19, the 1 in the sum being an input carry. The output of two decimal digits must be represented in BCD and should appear in the form listed in the columns. The 2 decimal digits, together with the input carry, are first added in the top 4-bit adder to produce the binary sum. An overflow detection circuit is used (to check if the 'Sum' of the BCD digit has exceeded 9).

SAMPLE TABLE:

A ₁	A ₂	A ₃	A ₄	B ₁	B ₂	B ₃	B ₄	S ₁	S ₂	S ₃	S ₄	C ₄	S ₁	S ₂	S ₃	S ₄	K
1	0	0	1	1	0	1	0	0	1	1	1	0	0	0	1	0	1

LOGIC DIAGRAM:

BCD ADDER

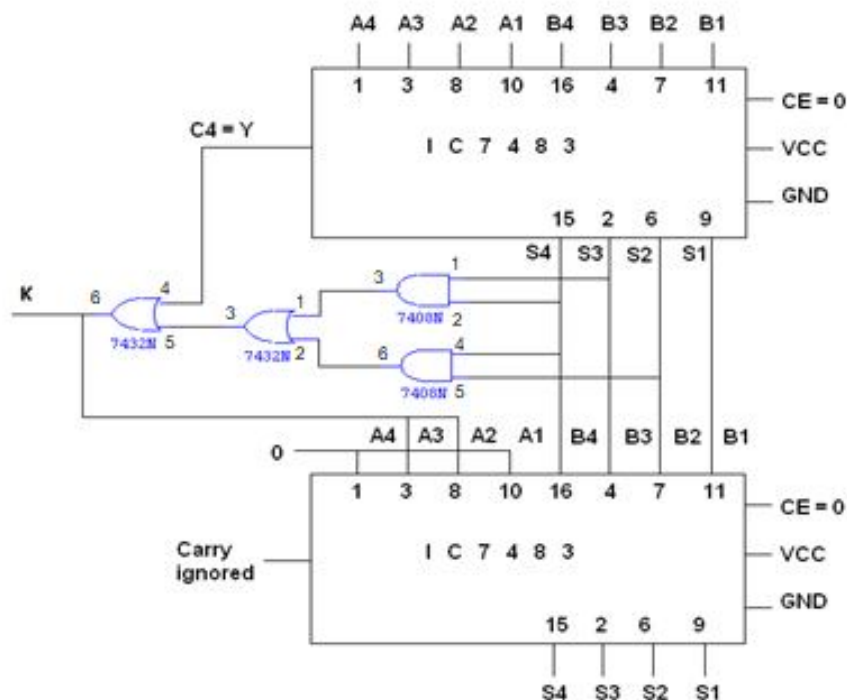

PROCEDURE:

- Connections are given as per circuit diagram.
- Logical inputs are given as per circuit diagram.
- Observe the output and verify the truth table.

OBSERVATION TABLE:

A ₁	A ₂	A ₃	A ₄	B ₁	B ₂	B ₃	B ₄	S ₁	S ₂	S ₃	S ₄	C ₄	S ₁	S ₂	S ₃	S ₄	K