

EXPT NO. : 12

AIM:

To demonstrate ALU or Arithmetic and Logical Unit as a digital circuit to perform several arithmetic operations using IC 74181.

APPARATUS REQUIRED:

Sl. No.	COMPONENT	SPECIFICATION	QTY.
1.	4-BIT ALU	IC 74181	1
3.	BREAD BOARD	-	1
4.	PATCH CORDS	-	-
4.	POWER SUPPLY WITH LOGIC PROBE	-	1

THEORY: ALU or Arithmetic and Logical Unit is a digital circuit to do arithmetic operations like addition, subtraction, division, multiplication and other logical operations.

Required functionality of ALU (inputs and outputs are active high)

Mode Select


F_n for active HIGH operands

Inputs				Logic	Arithmetic (note 2)
S3	S2	S1	S0	(M = H)	(M = L) ($C_n=L$)
L	L	L	L	A'	A
L	L	L	H	$A'+B'$	$A+B$
L	L	H	L	$A'B$	$A+B'$

L	L	H	H	Logic 0	minus 1
L	H	L	L	$(AB)'$	A plus AB'
L	H	L	H	B'	$(A + B)$ plus AB'
L	H	H	L	$A \oplus B$	A minus B minus 1
L	H	H	H	AB'	AB minus 1
H	L	L	L	$A'+B$	A plus AB
H	L	L	H	$(A \oplus B)'$	A plus B
H	L	H	L	B	$(A + B')$ plus AB
H	L	H	H	AB	AB minus 1
H	H	L	L	Logic 1	A plus A (Note 1)
H	H	L	H	$A+B'$	$(A + B)$ plus A
H	H	H	L	$A+B$	$(A + B')$ plus A
H	H	H	H	A	A minus 1

The L denotes the logic low and H denotes logic high.

ALU Logic Diagram:

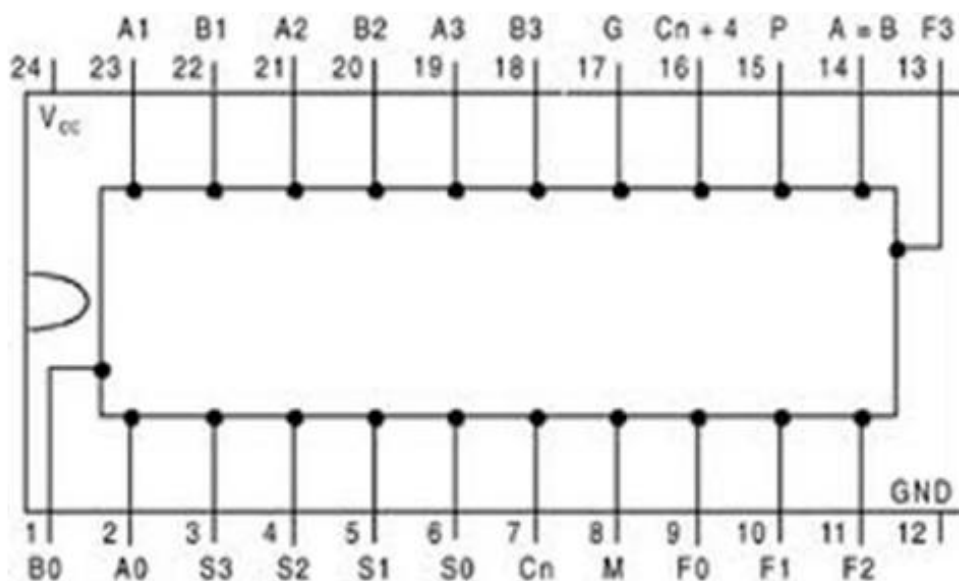

PROCEDURE:

- (iv) Connections are given as per circuit diagram.
- (v) Logical inputs are given as per circuit diagram.
- (vi) Observe the output and verify the truth table.

OBSERVATION TABLE:

A ₀	A ₁	A ₂	A ₃	B ₀	B ₁	B ₂	B ₃	C _n	S ₀	S ₁	S ₂	S ₃	F ₀	F ₁	F ₂	F ₃	M