

EXPT NO. : 6

## DESIGN AND IMPLEMENTATION OF MAGNITUDE COMPARATOR

**AIM:** To design and implement

- (i) 2 – Bit magnitude comparator using basic gates.
- (ii) 8 – Bit magnitude comparator using IC 7485.

### APPARATUS REQUIRED:

Sl. No.	COMPONENT	SPECIFICATION	QTY.
1.	AND GATE	IC 7408	2
2.	X-OR GATE	IC 7486	1
3.	OR GATE	IC 7432	1
4.	NOT GATE	IC 7404	1
5.	4-BIT MAGNITUDE COMPARATOR	IC 7485	2
6.	BREAD BOARD	-	1
7.	PATCH CORDS	-	-
8.	POWER SUPPLY WITH LOGIC PROBE	-	1

**THEORY:** The comparison of two numbers is an operator that determine one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determine their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$  (or)  $A < B$ .

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

The equality of the two numbers and B is displayed in a combinational circuit designated by the symbol (A=B).

This indicates A greater than B, then inspect the relative magnitude of pairs of significant digits starting from most significant position. A is 0 and that of B is 0.

We have  $A < B$ , the sequential comparison can be expanded as

$$A > B = A_3 B_3^1 + X_3 A_2 B_2^1 + X_3 X_2 A_1 B_1^1 + X_3 X_2 X_1 A_0 B_0^1$$

$$A < B = A_3^1 B_3 + X_3 A_2^1 B_2 + X_3 X_2 A_1^1 B_1 + X_3 X_2 X_1 A_0^1 B_0$$


The same circuit can be used to compare the relative magnitude of two BCD digits.

Where,  $A = B$  is expanded as,

$$A = B = (A_3 + B_3)(A_2 + B_2)(A_1 + B_1)(A_0 + B_0)$$

$$\begin{array}{ccc} \downarrow & \downarrow \downarrow & \downarrow \\ X_3 & X_2 \ X_1 & X_0 \end{array}$$

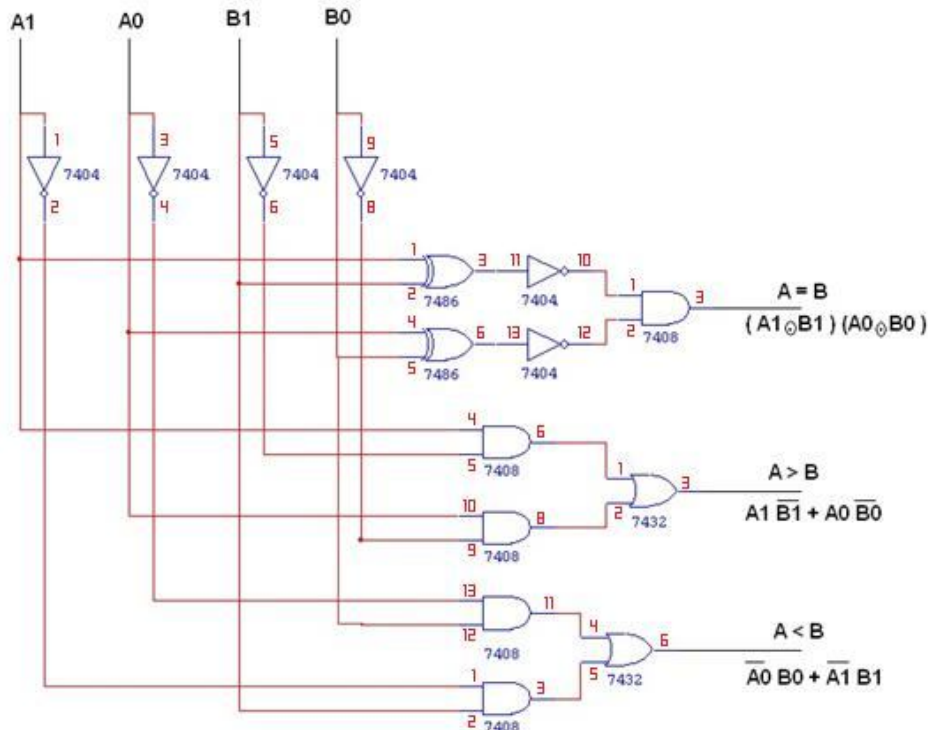
## LOGIC DIAGRAM: 2 BIT MAGNITUDE COMPARATOR




TRUTH TABLE:

A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	1	0	0	1	0	0

PIN DIAGRAM FOR IC 7485:

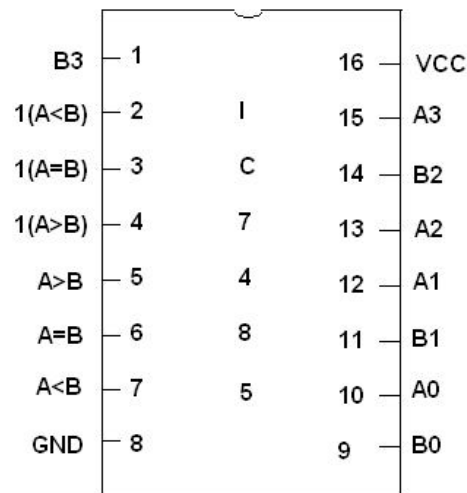

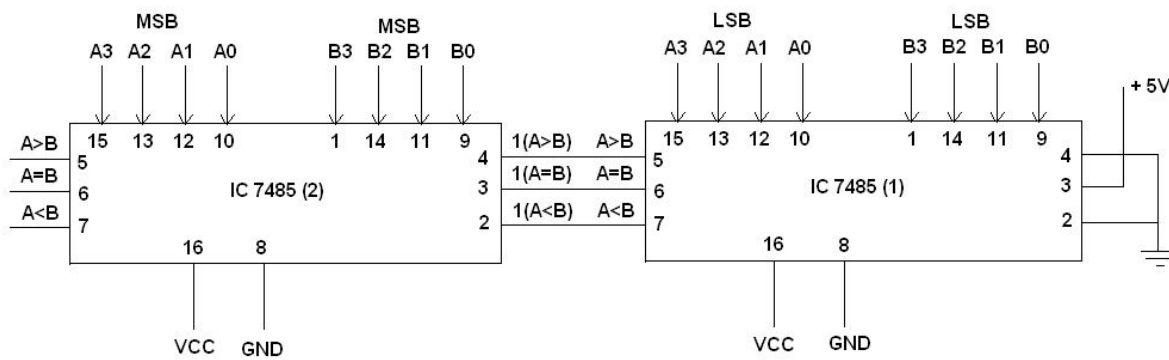LOGIC DIAGRAM: 8 BIT MAGNITUDE COMPARATOR



## TRUTH TABLE:

A	B	A>B	A=B	A<B
0000 0000	0000 0000	0	1	0
0001 0001	0000 0000	1	0	0
0000 0000	0001 0001	0	0	1

## PROCEDURE:

- Connections are given as per circuit diagram.
- Logical inputs are given as per circuit diagram.
- Observe the output and verify the truth table.

## OBSERVATION TABLE:

CIRCUIT	INPUTS		OUTPUTS		
	A	B	A>B	A=B	A<B
2-BIT MAGNITUDE COMPARATOR					
8-BIT MAGNITUDE COMPARATOR					