



EXPT NO. : 7

AIM:

Design of a 'Carry-Look- Ahead' Adder circuit


APPARATUS REQUIRED:

| Sl. No. | COMPONENT | SPECIFICATION | QTY. |
|---------|-------------------------------|---------------|------|
| 1. | X-OR GATE | IC 7486 | 1 |
| 2. | AND GATE | IC 7408 | 1 |
| 3. | OR GATE | IC 7432 | 1 |
| 4. | BREAD BOARD | - | 1 |
| 5. | PATCH CORDS | - | - |
| 6. | POWER SUPPLY WITH LOGIC PROBE | - | 1 |

THEORY:

To reduce the computation time, there are faster ways to add two binary numbers by using carry look ahead adders. They work by creating two signals P and G known to be **Carry Propagator** and **Carry Generator**. The carry propagator is propagated to the next level whereas the carry generator is used to generate the output carry, regardless of input carry.

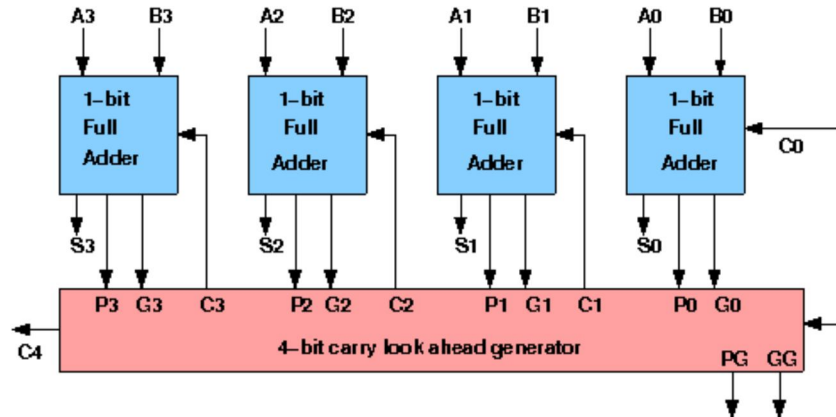The block diagram of a 4-bit Carry Look Ahead Adder is shown here below –



The number of gate levels for the carry propagation can be found from the circuit of full adder. The signal from input carry C_{in} to output carry C_{out} requires an AND gate and an OR gate, which constitutes two gate levels. So if there are four full adders in the parallel adder, the output carry C_5 would have $2 \times 4 = 8$ gate levels from C_1 to C_5 . For an n -bit parallel adder, there are $2n$ gate levels to propagate through. The corresponding boolean expressions are given here to construct a carry look ahead adder. In the carry look ahead circuit we need to generate the two signals carry propagator (P) and carry generator (G),

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

The output sum and carry can be expressed as

$$Sum_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + (P_i \cdot C_i)$$

Having these we could design the circuit. We can now write the Boolean function for the carry output of each stage and substitute for each C_i its value from the previous equations:

$$C_1 = G_0 + P_0 \cdot C_0$$


$$C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$

$$C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

CARRY LOOK AHEAD ADDER LOGIC DIAGRAM:

2 Bit CLA:

 

TRUTH TABLE:

| INPUT | | | | | OUTPUT | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A ₀ | B ₀ | C ₀ | A ₁ | B ₁ | S ₀ | S ₁ | C ₂ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

PROCEDURE:

- Connections are given as per circuit diagram.
- Logical inputs are given as per circuit diagram.
- Observe the output and verify the truth table.

OBSERVATION TABLE:

| INPUT | | | | | OUTPUT | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A ₀ | B ₀ | C ₀ | A ₁ | B ₁ | S ₀ | S ₁ | C ₂ |
| | | | | | | | |